
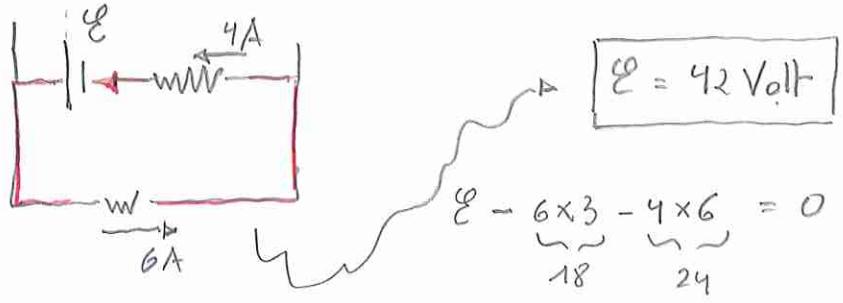


$I + 4 = 6 \text{ :-)}$

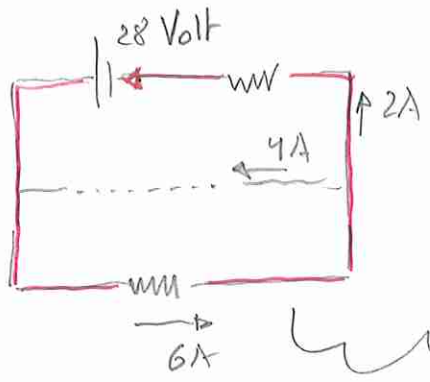


$E - \underbrace{6 \times 3}_{18} - \underbrace{4 \times 6}_{24} = 0$



$28 - \underbrace{6 \times 3}_{18} - 2 \times R = 0$

$R = 5\ \Omega$

CIRCUIT COUPE EN x :-)


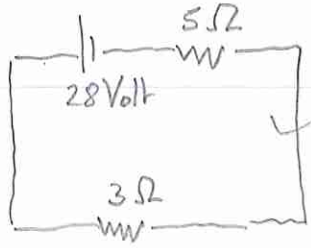


$28 - (5 + 3)I = 0$

$I = \frac{28}{8} = 3,5\text{ A}$

UNE SOURCE DE TENSION DISPARAIT
LE COURANT DIMINUE DANS LA RESISTANCE
DE 3 Ohm :-)


103

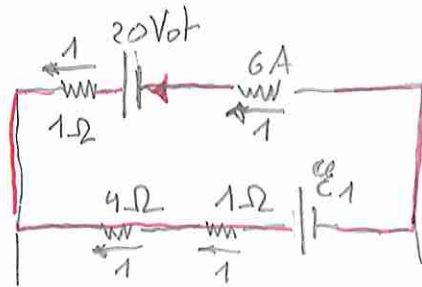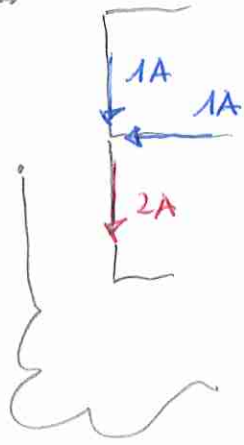

$$20\text{ Volt} - \underbrace{1 \times 1}_1 + \underbrace{(4+1) \times 1}_5 - E_1 - \underbrace{6 \times 1}_6 = 0$$

$$E_1 = 18\text{ Volt}$$

$$E_1 = 25 - 7 = 18\text{ Volt}$$

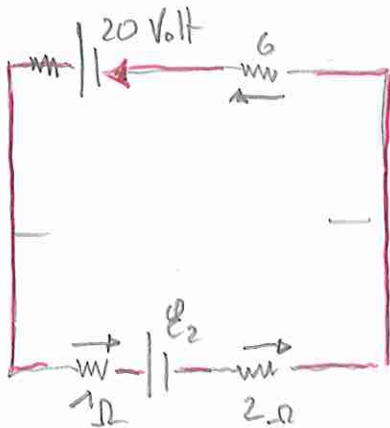


$$20 - \underbrace{(1 \times 2)}_2 - E_2 - \underbrace{(2 \times 2)}_4 - \underbrace{(6 \times 1)}_6 - \underbrace{(1 \times 1)}_1 = 0$$

$$E_2 = 20 - 13$$

$$E_2 = 7\text{ Volt}$$

104

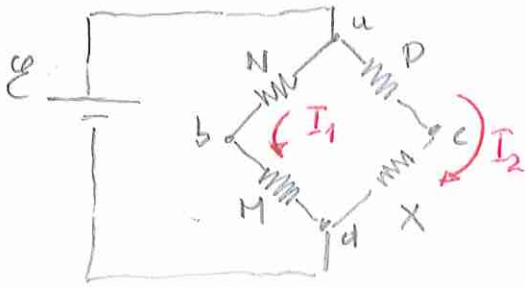

$$V_{eb} = V_{ac}$$

$$I_1 N = I_2 P$$

$$\begin{cases} \mathcal{E} = I_1(N+M) \\ \mathcal{E} = I_2(P+X) \end{cases}$$

$$\frac{N\mathcal{E}}{(N+M)} = \frac{P\mathcal{E}}{(P+X)}$$

$$N(P+X) = P(N+M)$$


$$NX = PM$$

$$X = \frac{MP}{N}$$

860, 33,38, 14

$$X = 2050 \Omega$$


105

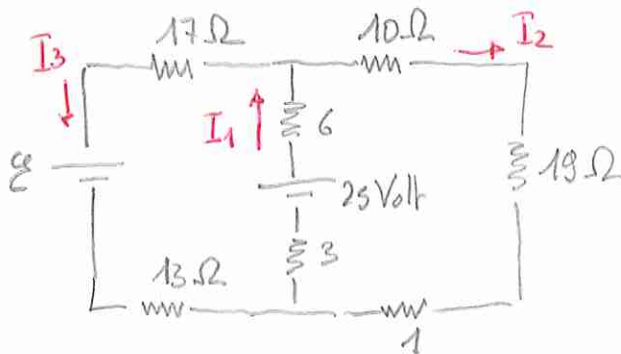

$$P = I_1^2 R$$

23, 6
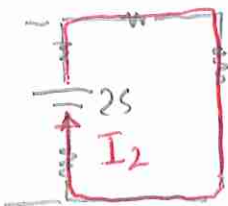
$$I_1 = \sqrt{\frac{23}{6}} = 1,96 \text{ A}$$



$$25 - \underbrace{(1,96)(6+3)}_{17,64} - \underbrace{(10+19+1)}_{30} I_2 = 0$$

$$I_2 = 0,245 \text{ A}$$

$$I_3 = 1,715 \text{ A}$$

$$25 - \underbrace{(1,96)(6+3)}_{17,64} - \underbrace{(1,715)(17+13)}_{51,45} - \mathcal{E} = 0$$


$$\mathcal{E} = -44,1 \text{ Volt}$$



LA POLARITE DE LA BATTERIE EST INVERSE A CELLE INDIQUEE SUR LE SCHEMA

106

$t=0$

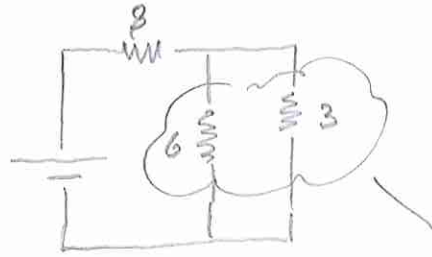

$$\frac{1}{6} + \frac{1}{3} = \frac{1}{R_{||}}$$

$$\frac{3}{6} = \frac{1}{R_{||}} \Rightarrow R_{||} = 2$$

$$\mathcal{E} = I(R + R_{||})$$


$$42 = I(2 + 8) \Rightarrow I = \frac{42}{10} = 4,2 \text{ A}$$

$$I(t) = \frac{V}{R} \exp(-t/RC)$$

$$I(0) = \frac{V}{R} \quad ; -)$$

$t \rightarrow \infty$

PLUS DE COURANT PAR LA CAPACITE !

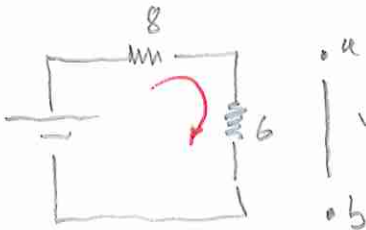

$$V_{ab} = \frac{6 \times 3}{18}$$


$$4 \cdot 10^{-6}$$

$$Q = C V_{ab}$$

$$\mathcal{E} = I(8 + 6) \Rightarrow I = \frac{42}{14} = 3 \text{ A}$$

$$Q = 72 \cdot 10^{-6} \text{ C}$$


107

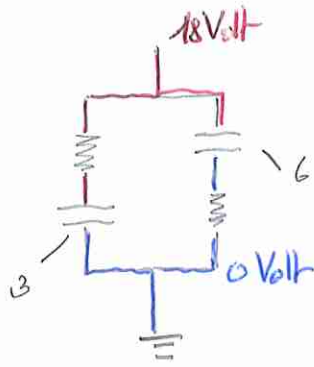

INTERRUPTEUR OUVERT

$$V_{ab} = 18 \text{ Volt } \therefore$$

a A LE POTENTIEL LE PLUS ELEVE !

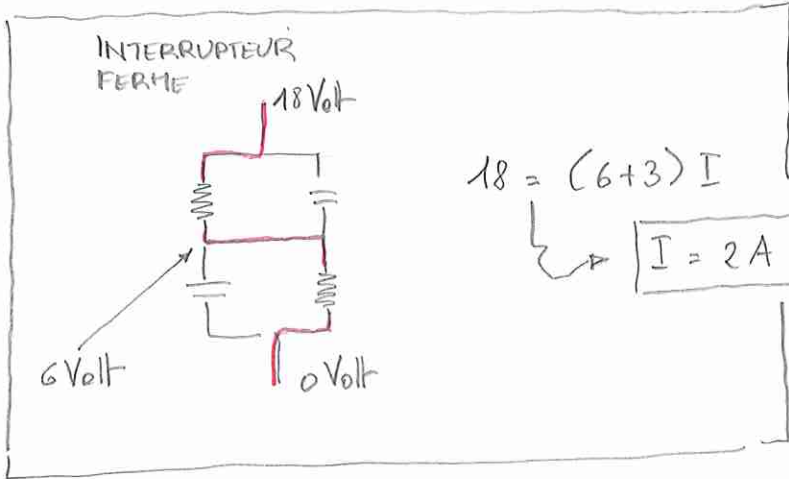

$$18 = (6+3) I$$

$$I = 2 \text{ A}$$

CHARGES INITIALES DE CONDENSATEURS

$$3 \cdot 10^{-6} \times 18 = 54 \cdot 10^{-6} \text{ C}$$

$$6 \cdot 10^{-6} \times 18 = 108 \cdot 10^{-6} \text{ C}$$

APRES AVOIR FERME L'INTERRUPTEUR

$$3 \cdot 10^{-6} \times 6 = 18 \cdot 10^{-6} \text{ C}$$

$$6 \cdot 10^{-6} \times 12 = 72 \cdot 10^{-6} \text{ C}$$

PERTE DE CHARGES DES 2 CONDENSATEURS

$$36 \cdot 10^{-6} \text{ C}$$

$$36 \cdot 10^{-6} \text{ C}$$

C'EST LOGIQUE LE VOLTAGE DIMINUE AUTOUR DES DEUX CONDENSATEURS.

108

$$R = \frac{\rho L}{\pi R^2}$$

10^{11} $12 \cdot 10^{-9}$ $0,09 \cdot 10^{-18}$

$$\rho = \frac{\pi \cdot 0,09 \cdot 10^2}{12}$$

$$\rho = 2,4 \text{ } \Omega \cdot \text{m}$$

$$\sum_{i=1}^n \frac{1}{R} = \frac{n}{R} = \frac{1}{R_{eq}}$$

$$R_{eq} = R/n$$

$$V = \frac{R I}{n} \quad \left\{ \begin{array}{l} \text{ } \\ \text{ } \end{array} \right. \text{ } \mu \text{A}$$

$$\frac{n}{A} = \frac{R I}{V} = \frac{10^{11} [\Omega] \cdot 5 [\mu\text{A}/\text{cm}^2]}{50 [\mu\text{Volt}]}$$

$$= 10^{10} [1/\text{cm}^2]$$

$$\frac{n}{A} = 100 [1/\mu\text{m}^2]$$

$$\tau = RC = \underbrace{10^{11}}_{10^{-5}} \times \underbrace{10^{-16}}_{10^{-5}} = 10^{-5} [\text{s}]$$